


STM32F103C8T6 Development Board

*Custom PCB
Design & Layout
with*

STM32F103C8T6
microcontroller

*A beginner-friendly dev
board featuring USB, SWD,
UART, and I2C interfaces.
Designed and routed
entirely in KiCad.*

**Designed by
Nithil A Rao**

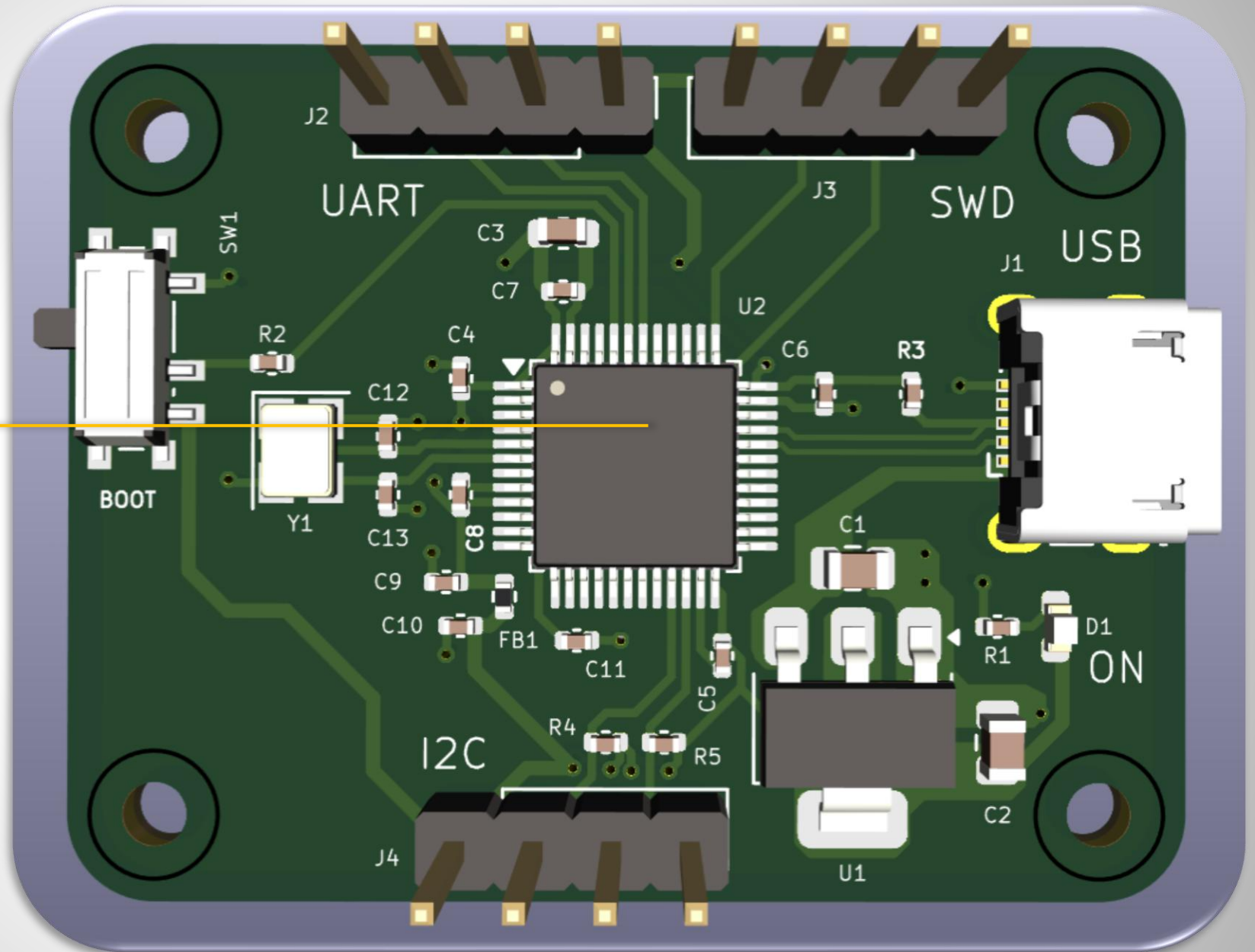





Schematic

Power Supply


The diagram illustrates a power supply circuit. It features a USB input with VBUS and GND pins. A capacitor C1 (22uF) is connected across the input. The VBUS line passes through a diode D1 (RED) and a resistor R1 (1k5) to a PWR_LED_K. The GND line passes through a capacitor C2 (22uF) to a +3.3V output. The diode D1 is connected between the +3.3V output and the PWR_LED_K. The component U1 is labeled AMS1117-3.3.

VBUS from USB connector (normally +5V)
Min 22uF I/O capacitors

-  H1
 Mounting Hole
 H2
 Mounting Hole
 H3
 Mounting Hole
 H4
 Mounting Hole


Nithil A Rao




Microcontroller(and USB)

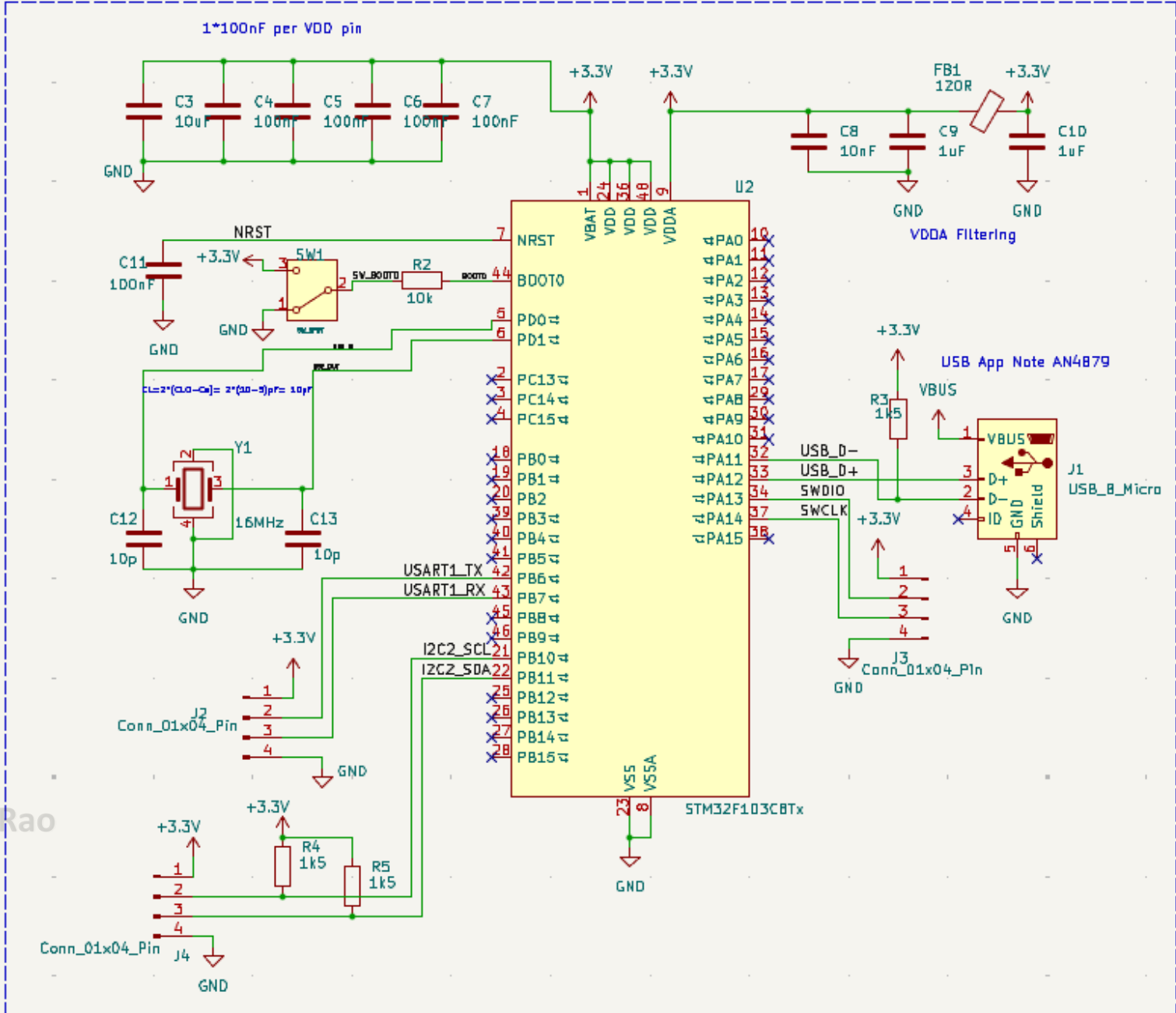

PIN-out using STM32Cube IDE

Layout

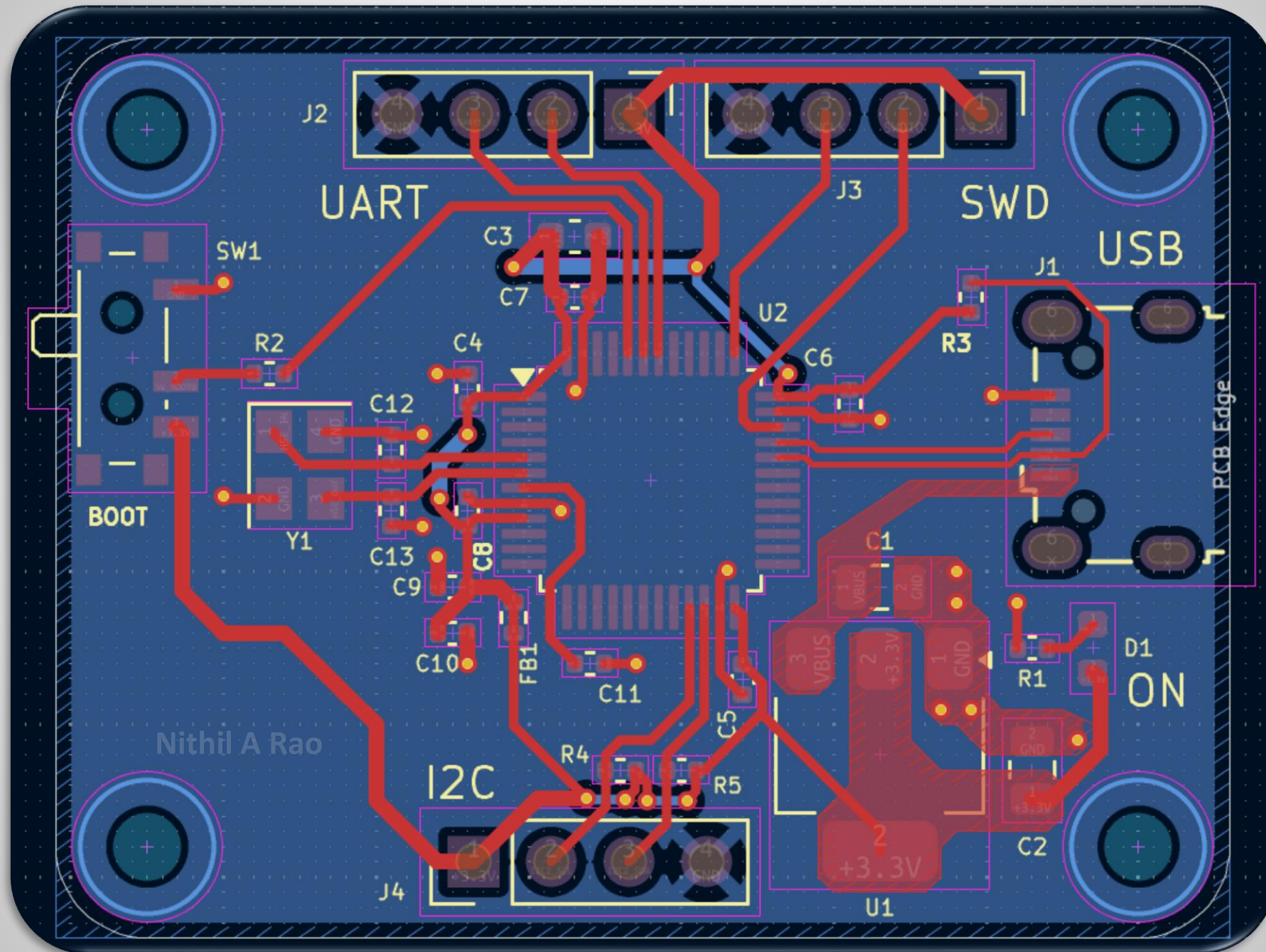


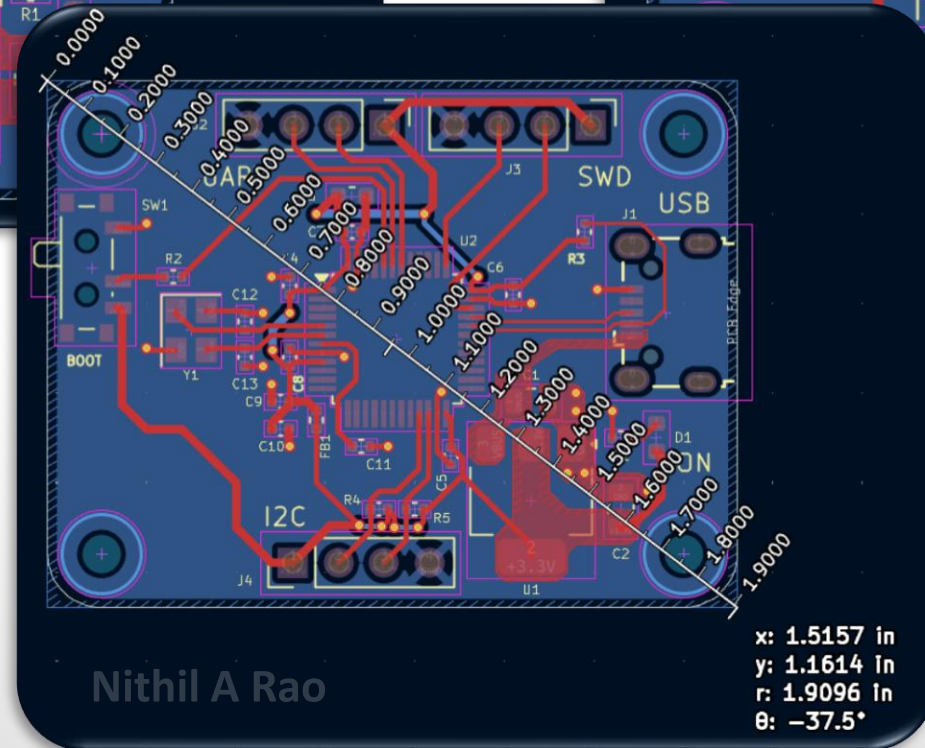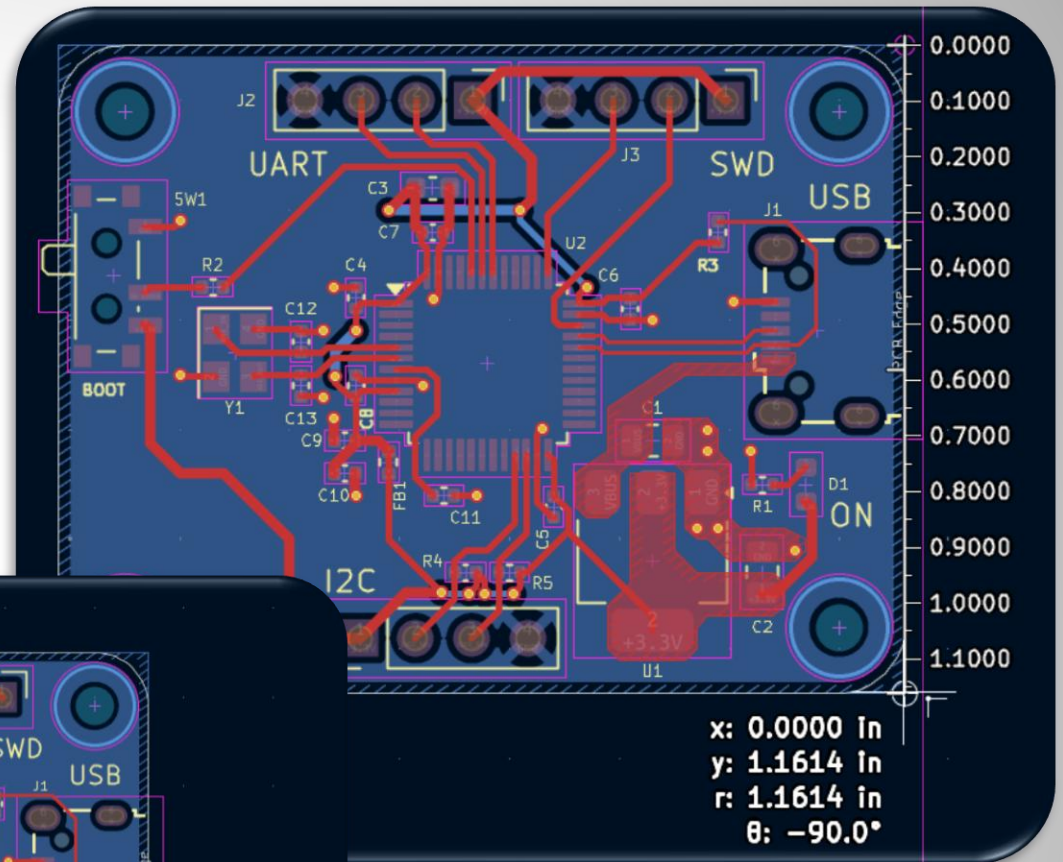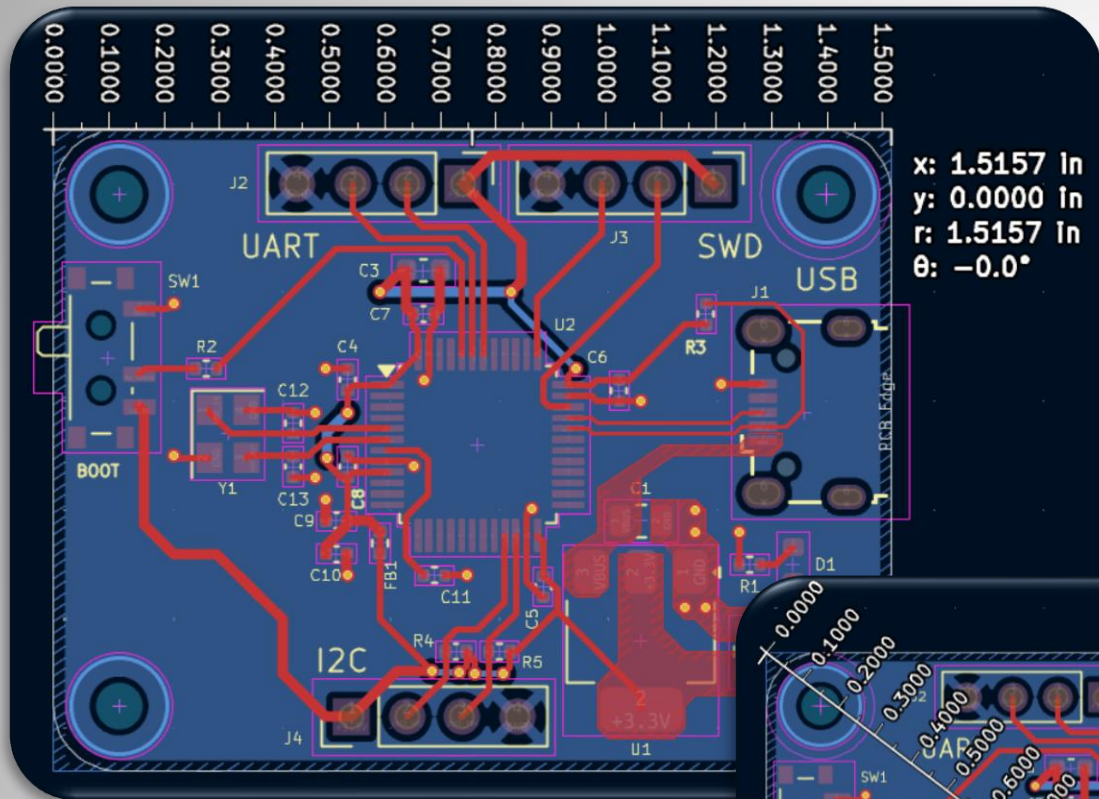


Dimensions

Nithil A Rao

Front

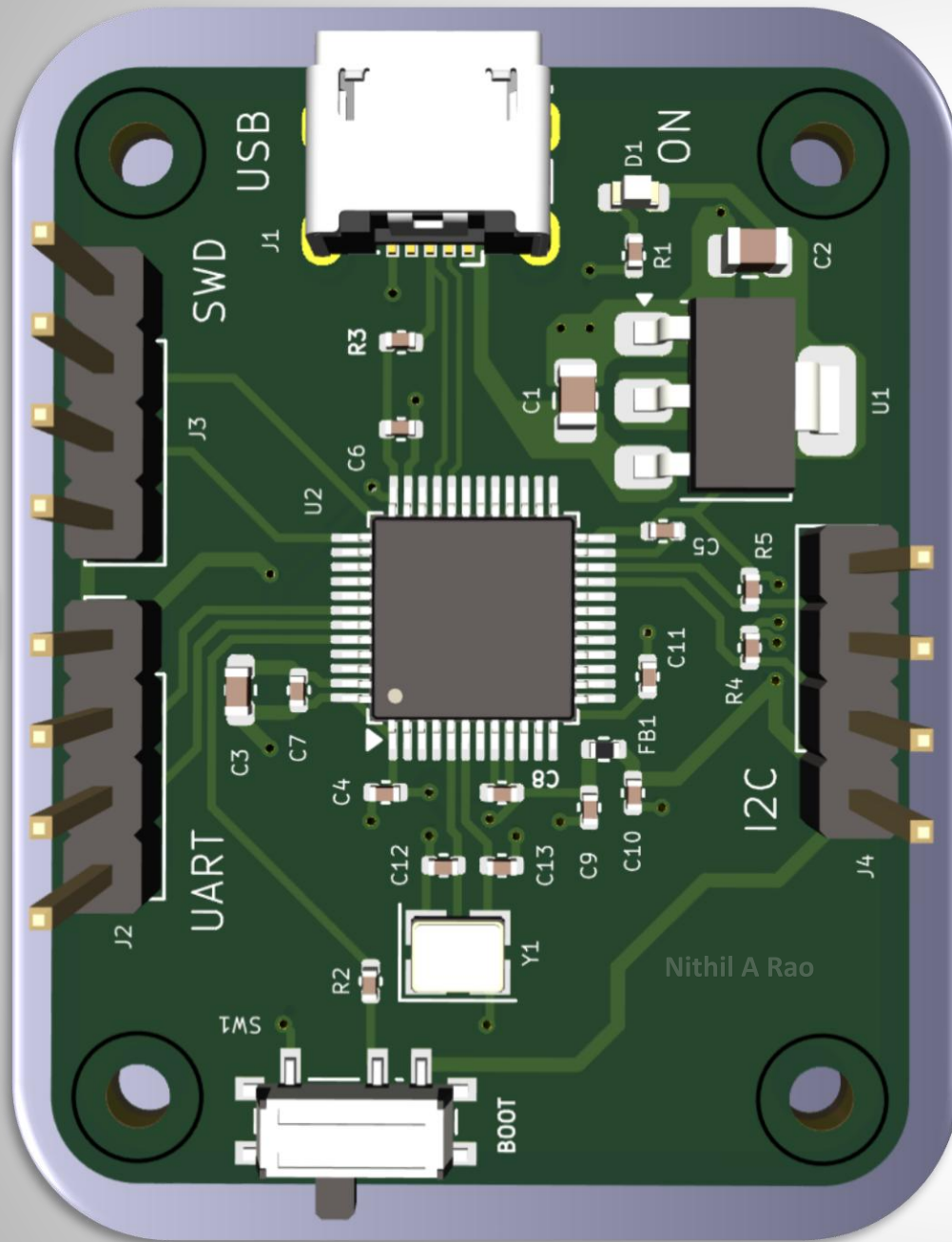


Back

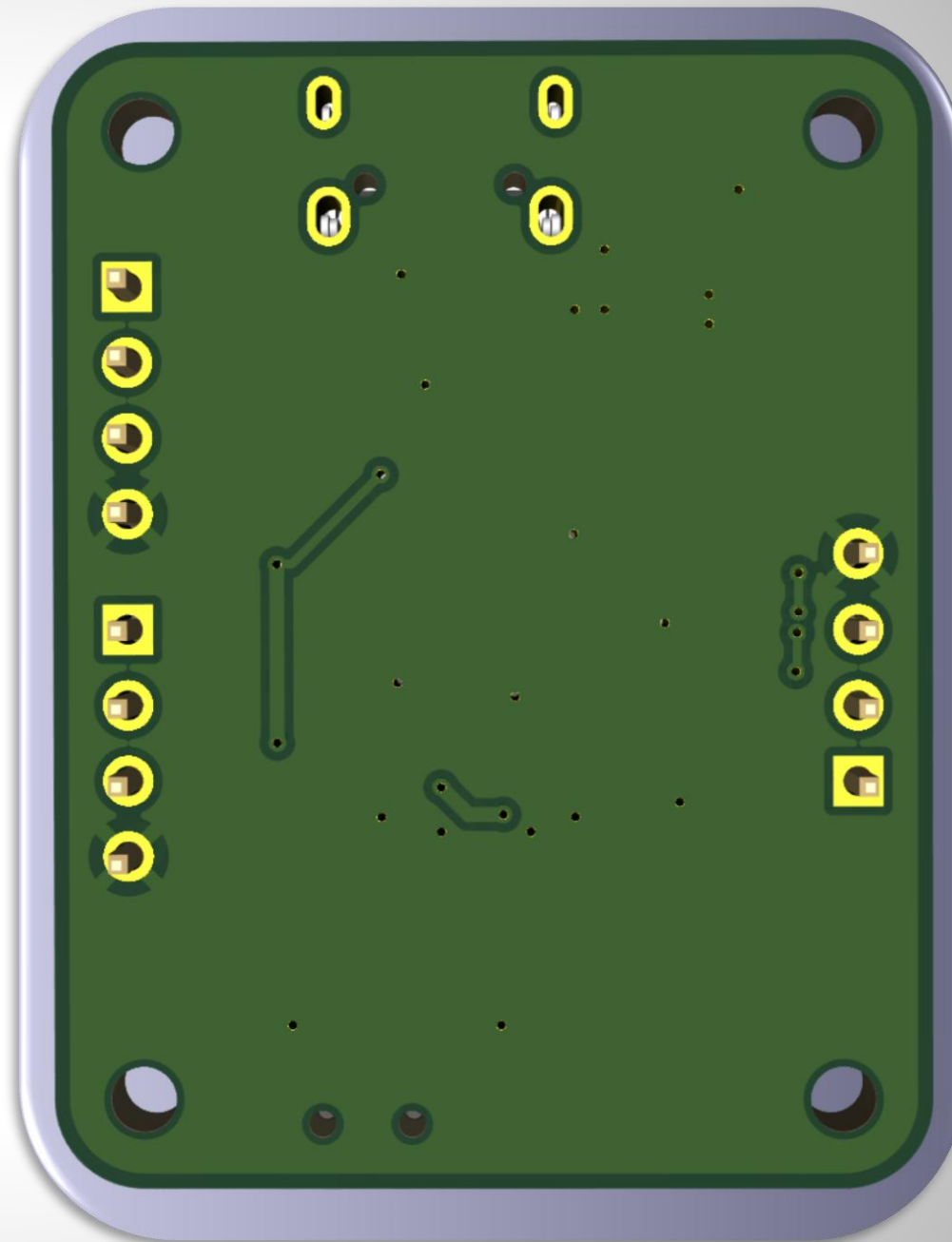


Power Supply Design

Used a **linear regulator** to convert input voltage (e.g., 5V) to 3.3V.

Power Supply


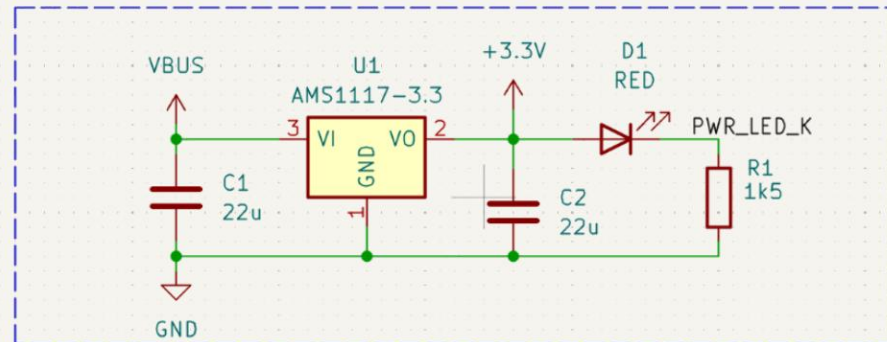


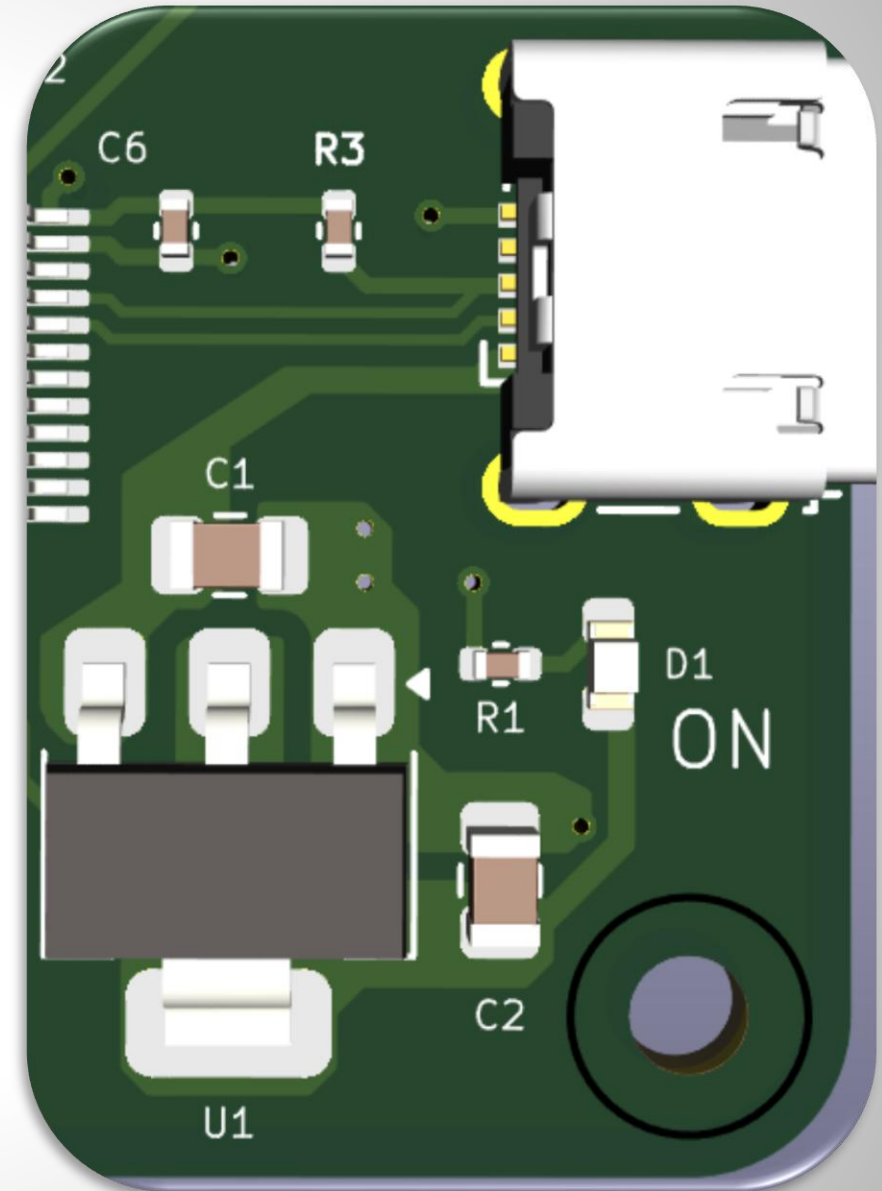VBUS from USB connector (normally +5V)
Min 22µF I/O capacitors






Crystal Oscillator Circuit

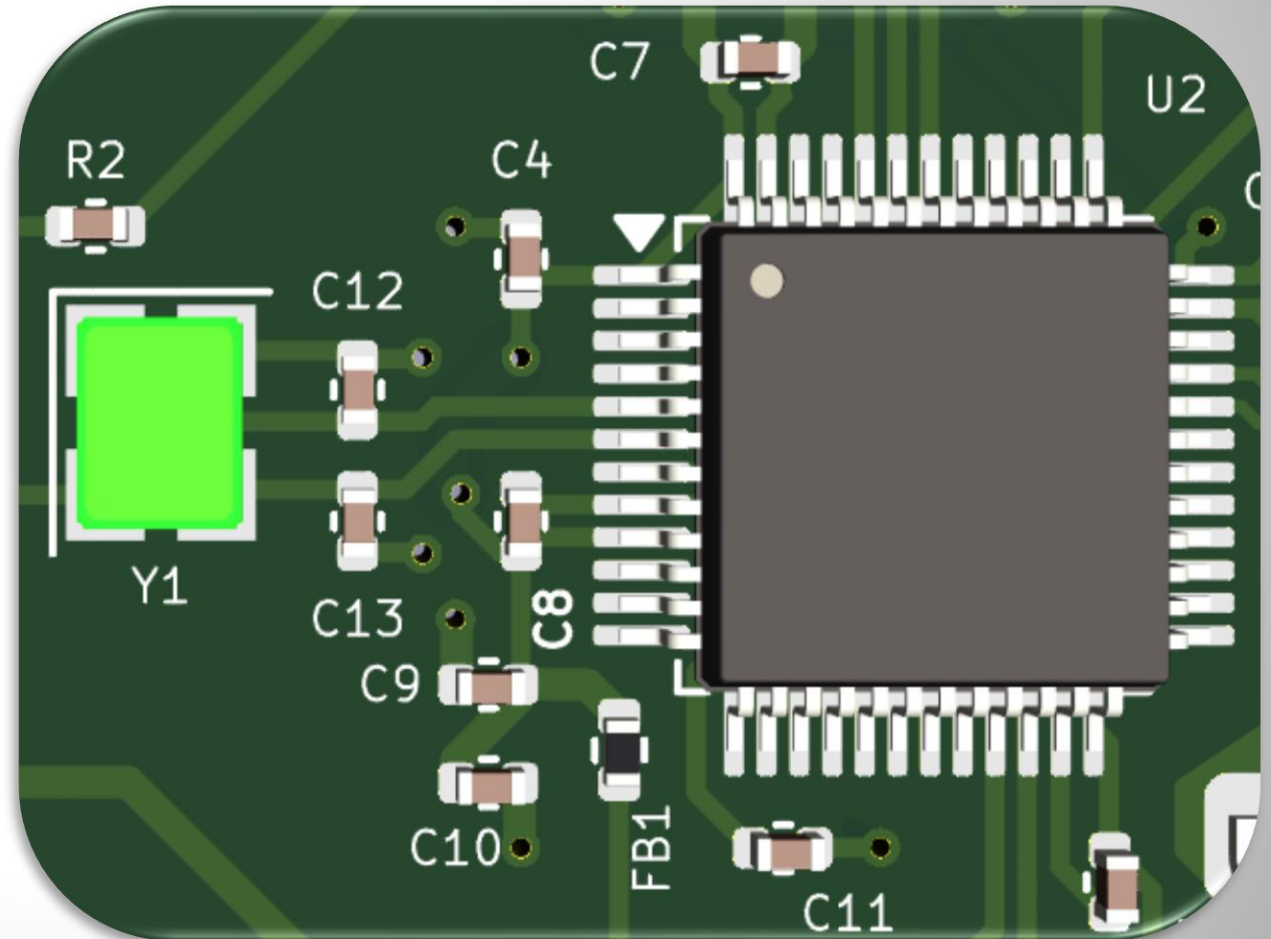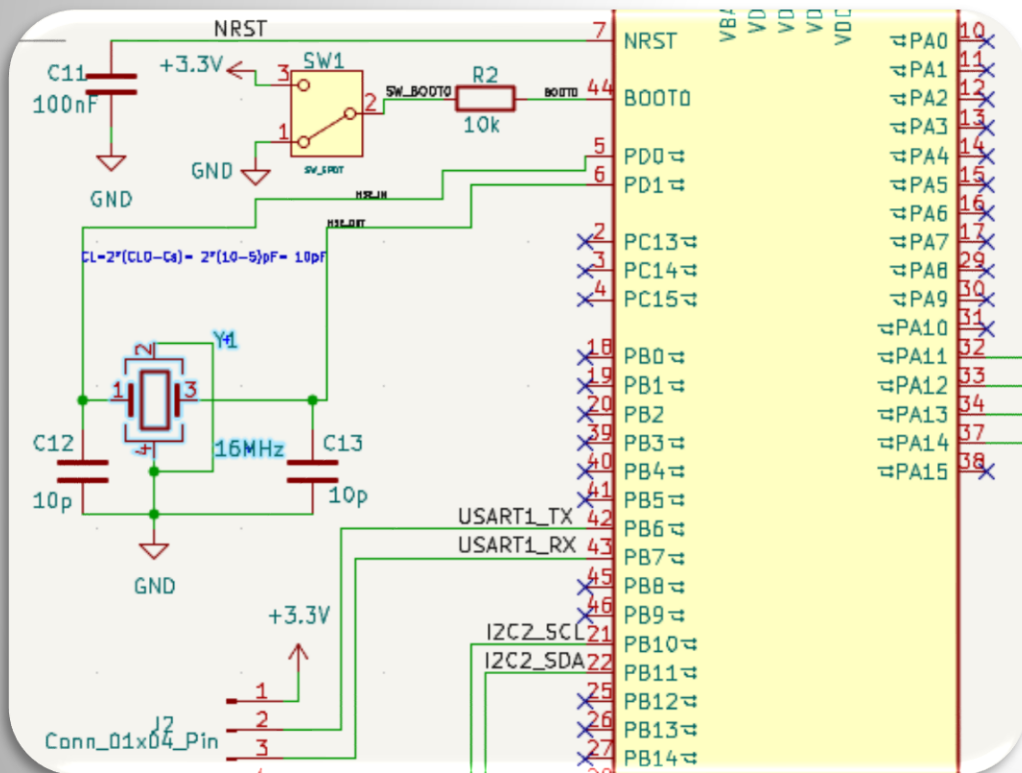Provides a stable clock source for the microcontroller's timing functions.




Solid Pads

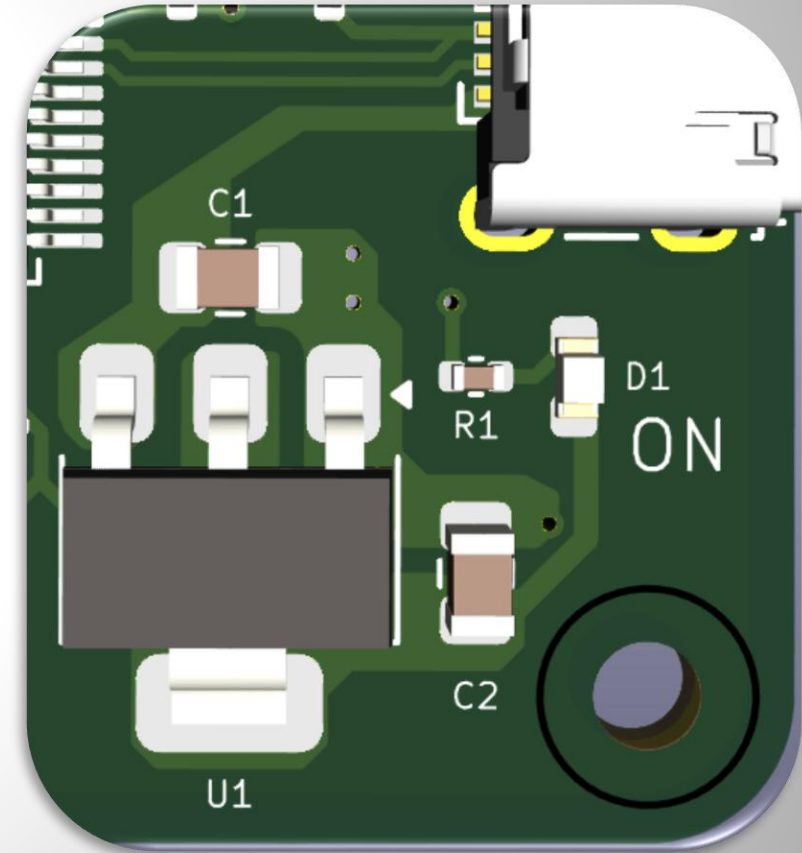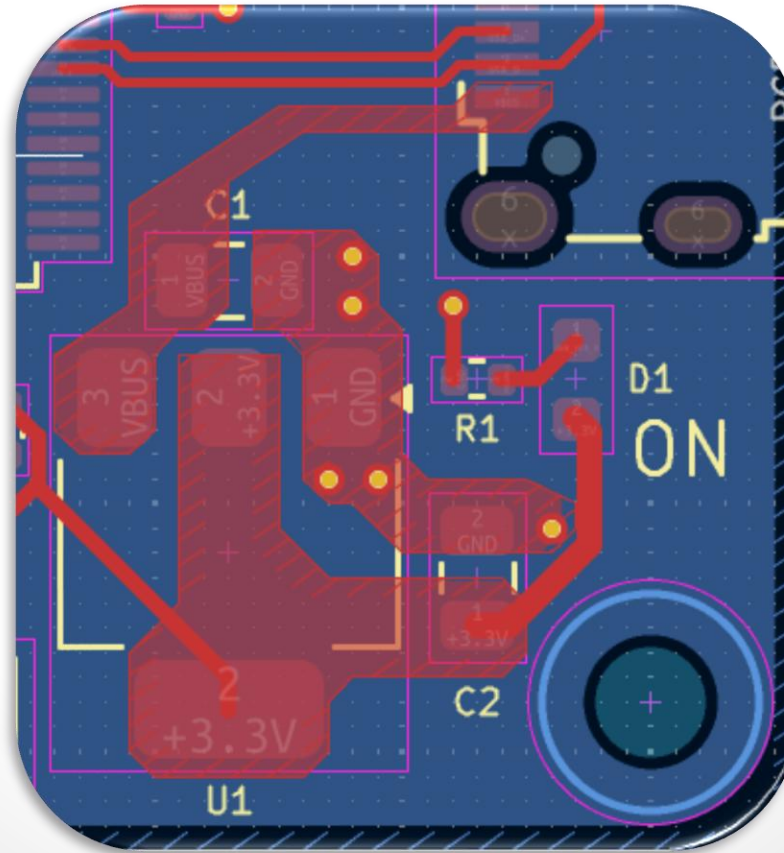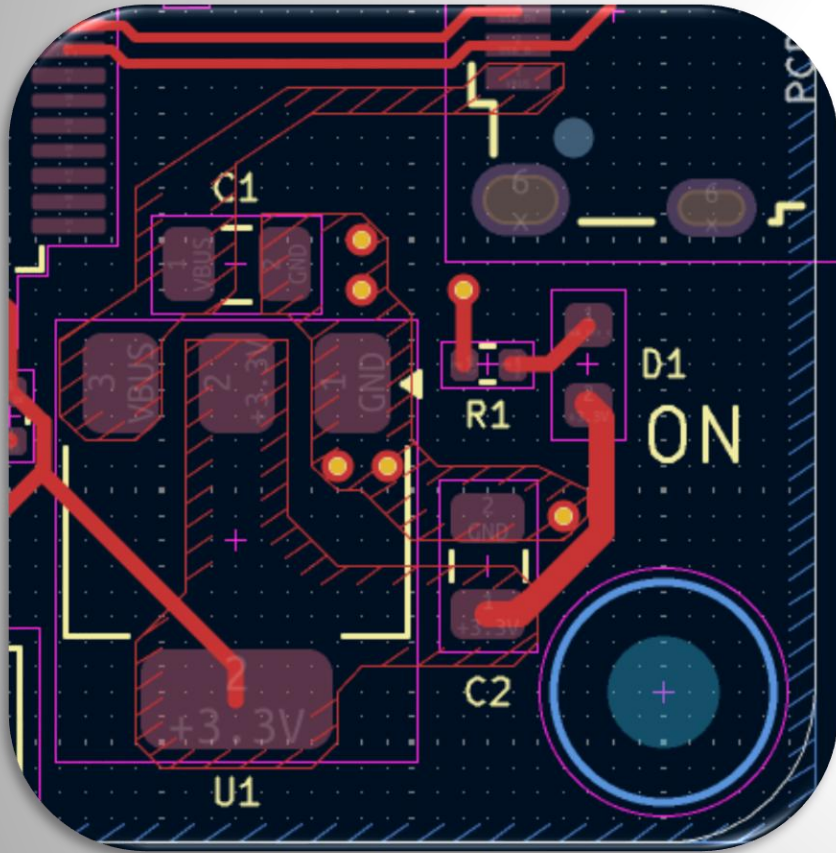Used to bridge multiple signal lines/components with copper. Easier than routing separate traces.



Decoupling & Filtering

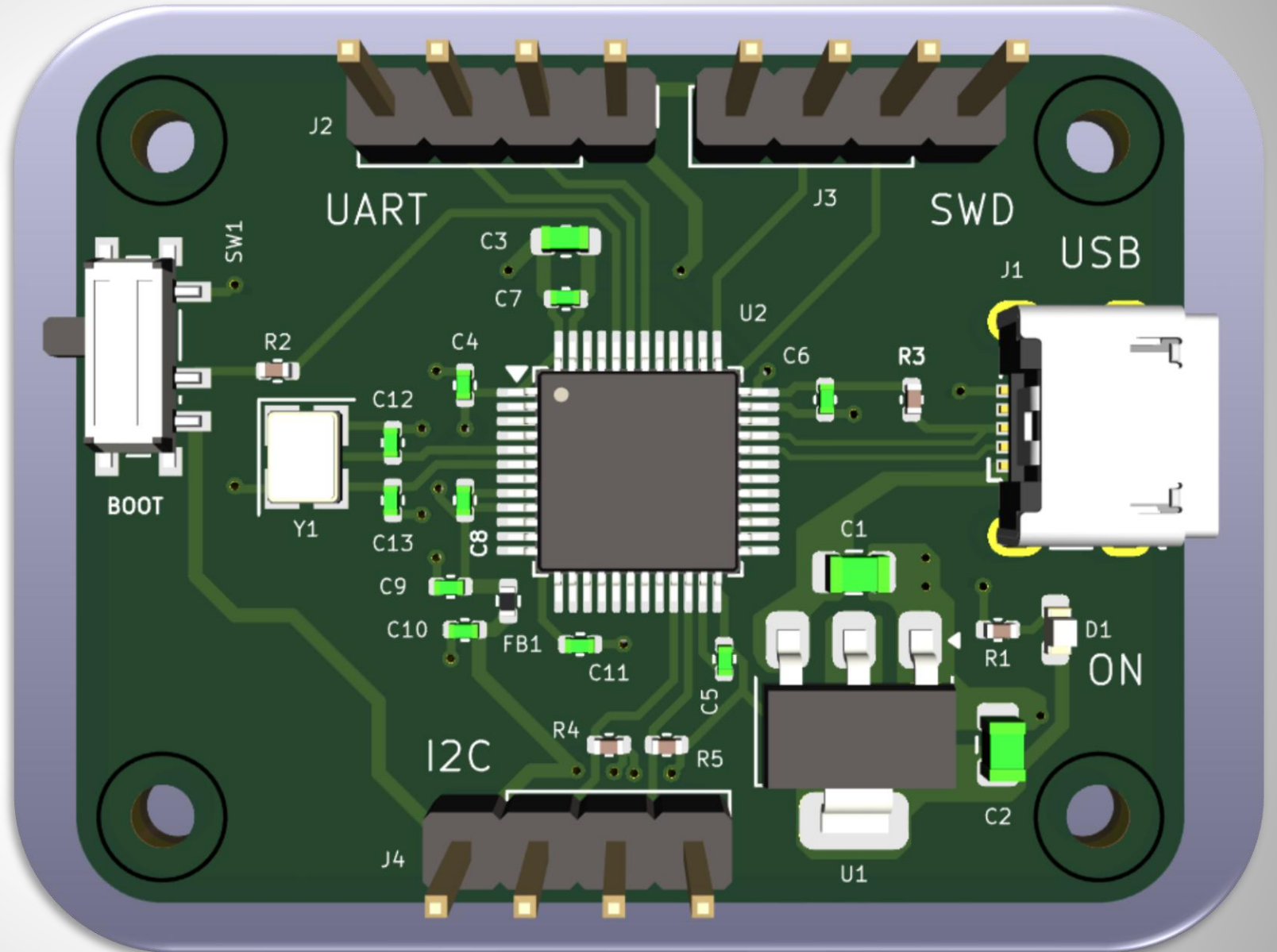- **Decoupling capacitors** placed close to MCU pins reduce noise and stabilize voltage.
- **Ferrite beads** separate analog and digital power domains to reduce high-frequency noise.



Project Learnings

- Decoupling capacitors placed close to the MCU to reduce voltage ripple and noise
- USB D+ and D- routed as a differential pair with equal length for signal integrity
- Solid copper pads used to bridge terminals cleanly and reduce routing clutter
- Unused MCU pins either grounded, pulled up/down, or marked as NC to avoid noise
- SWD interface added for debugging and flashing firmware
- BOOT0 switch included to enter USB bootloader mode
- UART header for serial communication
- I2C pins with pull-up resistors for sensor/module communication
- Crystal provides accurate clock; load caps stabilize oscillation